

AND : Returns True if both conditions are True

OR : Returns True if at least one of the conditions are True

NOT : Inverts the Boolean value. It Returns True if the original condition is False. Returns False if the original condition is True.


| A | B | A <u>AND</u> B |
|---|---|----------------|
| T | T | |
| T | F | |
| F | T | |
| F | F | |

| A | B | A <u>OR</u> B |
|---|---|---------------|
| T | T | |
| T | F | |
| F | T | |
| F | F | |

| A | <u>NOT</u> A |
|---|--------------|
| T | |
| F | |

①

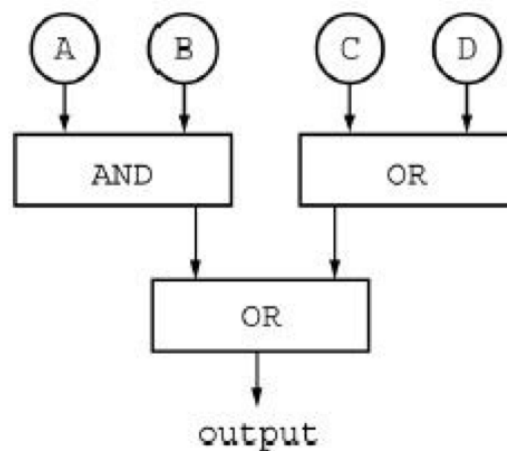
The diagram below shows a circuit composed of three logic gates. Each gate takes two inputs and produces a single output.



For which of the following input values will the circuit have an output of **true** ? (Select all)

- (A) A = true, B = false, C = false, D = false
- (B) A = true, B = true, C = false, D = false
- (C) A = false, B = false, C = true, D = true
- (D) A = false, B = false, C = false, D = true

2

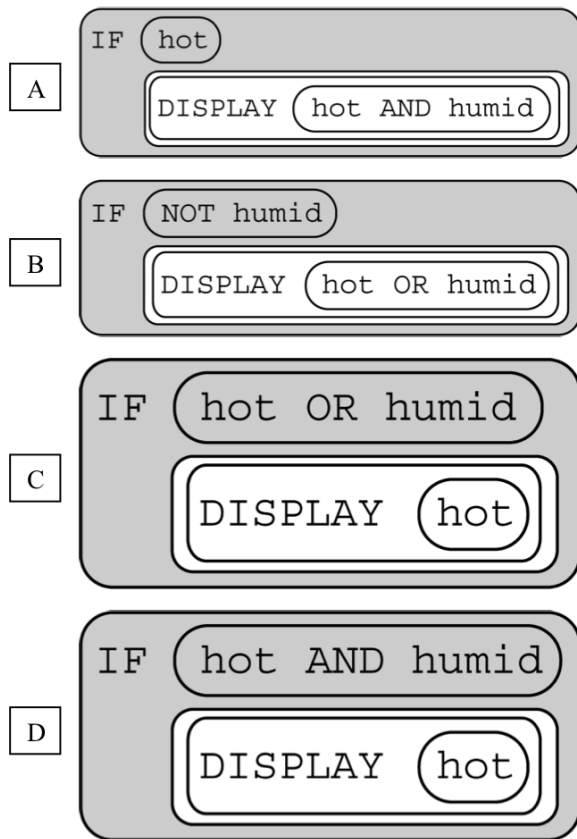

hot \leftarrow true
humid \leftarrow true

which will display
"true"?
(select all)

3

The following code segment is used to determine whether a customer is eligible for a discount on a movie ticket.

```
val1  $\leftarrow$  (NOT (category = "new")) OR (age  $\geq$  65)  
val2  $\leftarrow$  (category = "new") AND (age < 12)
```

If category is "new" and age is 20, what are the values of val1 and val2 as a result of executing the code segment?

val1 =
val2 =

If category is "new" and age is 65, what are the values of val1 and val2 as a result of executing the code segment?

val1 =
val2 =